

locktronics

Simplifying Electricity

Three phase systems



LK2686

MATRIX

www.matrixtsl.com

Copyright © 2014 Matrix Multimedia Limited

Contents


Introduction to Three-phase Power

	Introduction	3
Worksheet 1	- Single-phase AC	8
Worksheet 2	- Three-phase AC	10
Worksheet 3	- Phase basics	12
Worksheet 4	- And now the phasor	14
Worksheet 5	- It's a star	16
Worksheet 6	- On the delta	18
Worksheet 7	- Half-wave rectification	20
Worksheet 8	- Full-wave rectification	22
Worksheet 9	- Delivering power	24
	Instructor Guide	26

Introduction

Introduction to Three-phase Power

The hardware:

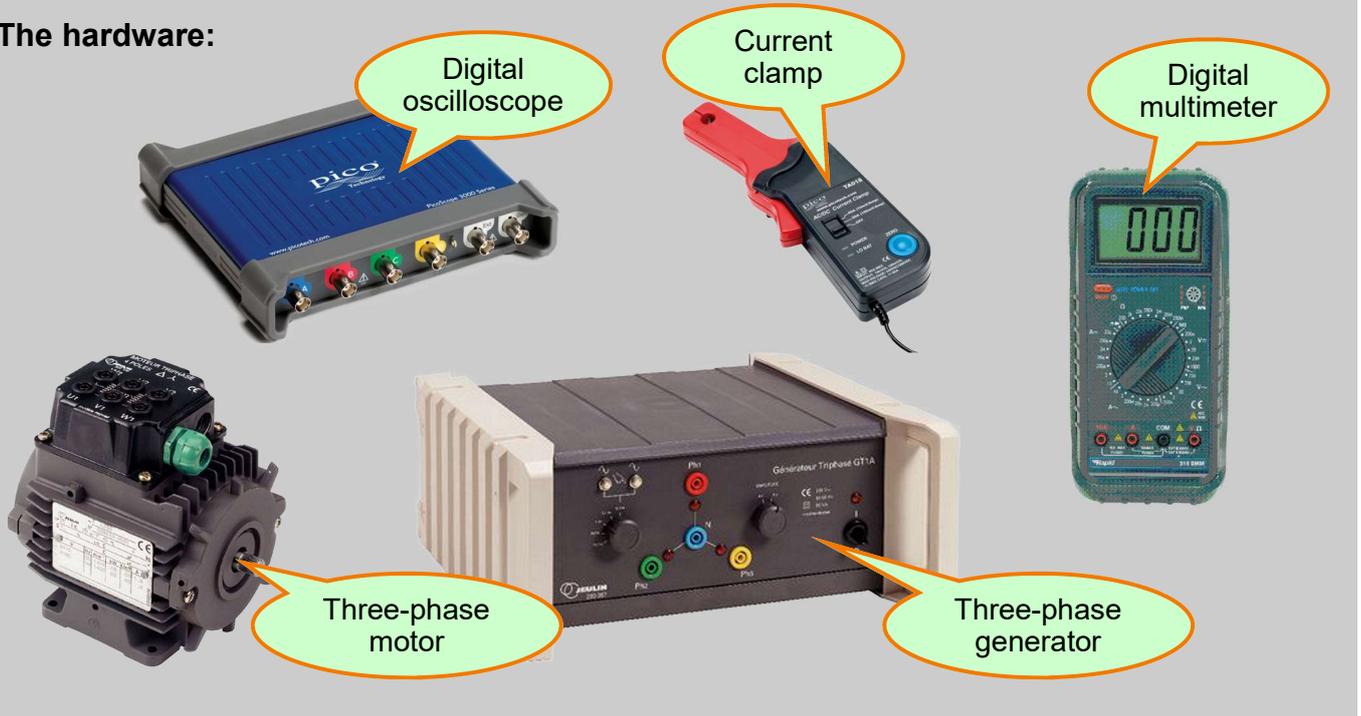

The hardware:

Three-phase generator

- converts single-phase AC mains into three phases. These can behave as three separate sources of AC power, or can be linked as one source.

Three-phase motor

- contains three independent sets of coils, each of which uses an AC supply to produce a rotating magnetic field inside the motor. This creates torque which makes the motor's rotor rotate.

Digital oscilloscope

- is used to study the AC signals involved in the three-phase systems;
- can create image files that record these signals for later analysis, or as records of the behaviour of the three-phase systems.

Current clamp

- generates a voltage that reflects the size and direction of the AC current;
- is connected to the digital oscilloscope, which displays voltage/time graphs, but cannot display AC current directly.

Multimeter

- measures voltage, current, resistance and a range of related quantities;
- cannot 'follow' rapidly changing signals;
- displays rms (root-mean-square) values of AC quantities usually.

Introduction

Introduction to Three-phase Power


Using the hardware

Three-phase generator

- has controls that allow the user to adjust:
 - signal amplitude, to 6V or 9V;
 - signal frequency, to 0.1Hz (variable), 0.1Hz fixed, 1 Hz, 50Hz and 150Hz;
- has red, green and yellow sockets for the three phases, and blue for the neutral connection;
- can deliver currents up to 0.8A from each phase;
- has LEDs on each phase that indicate overloads or short-circuits.

Three-phase motor

- has three sets of coils, **U**, **V** and **W**, that use the three-phase signals to produce rotating magnetic fields. Each creates four magnetic poles (two 'north' and two 'south'), and so it is known as a four-pole motor;
- has a squirrel-cage rotor in which currents are induced by the rotating magnetic fields;
- can operate as a single-phase motor (see worksheet 4);
- has a stroboscopic disc to facilitate measurement of rotational speed.

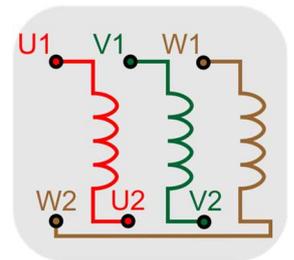

Digital oscilloscope

- monitors signals, usually time-varying, and presents its results as a voltage / time graph.
- digital oscilloscopes use digital processing techniques to obtain the results.

(Any oscilloscope can be used for this course, though at times, it needs to monitor four signals simultaneously. Further instructions on using the Picoscope are given later.)

Current clamp

- has a handle to open the jaws so they can be clamped around the wire carrying the current;
- can be used on AC and DC currents;
- produces an output voltage proportional to the current;
- has two ranges - 1mV/10mA and 1mV/100mA, allowing measurement up to 20A and 60A;
- has a switch to select the ranges (and on/off.)

Multimeter

- For voltage measurement:
 - plug probes into 'V Ω Hz' (or equivalent,) and 'COM';
 - select the range, either AC or DC;
 - connect the probes in parallel with the device under test.
- For current measurement:
 - plug probes into 'mA' or '10A' (or equivalent) and 'COM';
 - select the range, either AC or DC;
 - break the circuit just before or just after the device under test and connect the probes to each end of the break;
 - (No reading may mean that the internal fuse has 'blown'.)

Introduction to Three-phase Power

Power considerations:

In elementary science and engineering, electrical power, P , is calculated using the formula:

$$P = \text{current } I \times \text{voltage } V$$

In DC circuits, there is no problem. Steady currents involve only resistors, where voltage and current are in phase. When a current flows, the resistor dissipates energy and gets hot.

In AC circuits, however, current and voltage may not be in phase.

- In capacitors, current 'leads' voltage with a phase difference of 90° .
- In inductors, voltage 'leads' current with a phase difference of 90° .

As the formula above suggests, to deliver power requires both a voltage and current. In the graphs that follow, when voltage and current are both positive or both negative, the power is a positive quantity. We say that power is delivered to the circuit. When one is positive and the other negative, the power is negative - we say that power returns to the supply.

In the resistor graph, voltage and current are in phase always. It doesn't matter which way the

current flows, the resistor gets hot!


Power is delivered to the resistor all the time.

The capacitor graph shows that the current falls as the voltage across the capacitor rises. When the current reverses, the capacitor discharges and the voltage across it falls. Although there is both voltage and current at all times, sometimes energy is delivered **to** the capacitor to build up the electric field, and sometimes, it is released **back** to the circuit, as the field collapses. As these are identical, the **nett** power delivered is zero.

In the inductor graph, once a voltage is applied, a current builds up slowly. In the process, energy is stored in the inductor's magnetic field. When voltage and current reverse, the energy is returned to the supply. Once again, the nett power delivered is zero.

The bottom graph shows the situation in a complex circuit, i.e. one containing both resistive and reactive components. Now, the phase angle is somewhere between 0° and 90° .

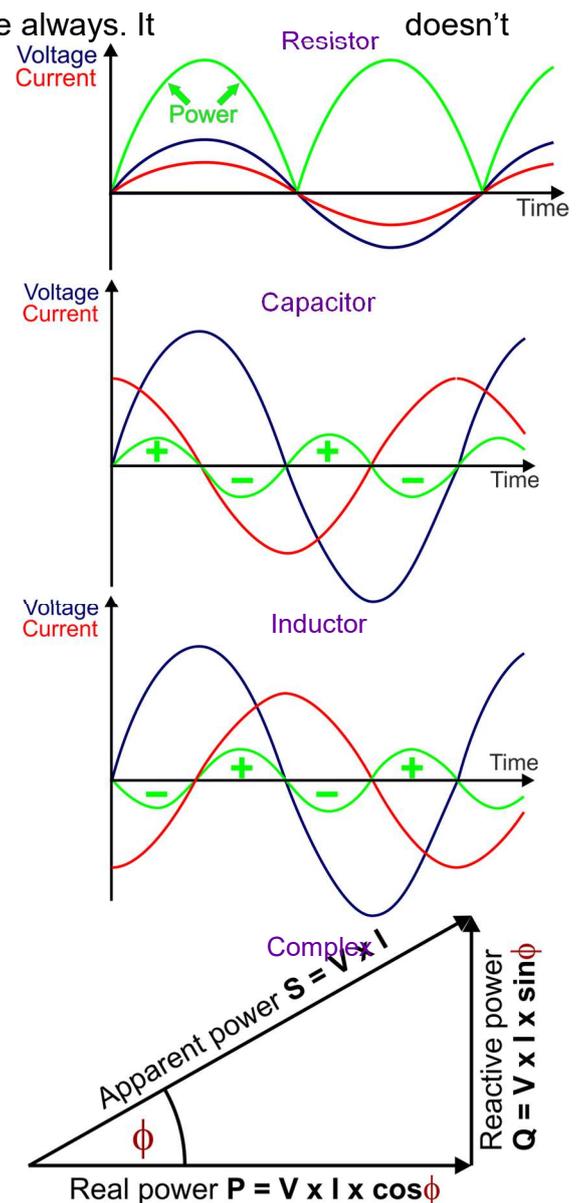Nett power is now delivered to the circuit.



Introduction

Introduction to Three-phase Power

Power considerations continued...:

In AC circuits, the issue of phase difference gives rise to three different measures of electrical power:

Real (or true, or active) power:

The only circuit elements that actually dissipate power are those with resistance, **R**. This real power **P**, measured in watts (W), is calculated using the formulae:

$$P = I^2 R \quad P = V^2 / R$$

(I = rms current, V = rms voltage)

Reactive power:

is the 'imaginary' power, **Q**, measured in 'volt-amp-reactive' (VAR), delivered to components with reactance, X, i.e. capacitors and inductors. It is calculated using :

$$Q = I^2 X \quad Q = V^2 / X$$

Although apparently useless, as it delivers zero nett power to purely reactive loads, it still flows through the circuit and so the cables etc. must be capable of handling it.

Apparent power:

Apparent power, **S**, measured in 'volt-amperes' (VA), is the total of real and reactive power - the power that the AC supply **seems** to be delivering to the load, of impedance Z.

It can be calculated using:

$$S = I^2 Z \quad S = V^2 / Z$$

or

$$S = I \times V$$

The relative sizes of these three measures depends on the 'power factor' of the circuit.

Power factor:

In an AC circuit, current, **I**, may be out of phase with voltage, **V**, by a phase angle ϕ .

The diagram shows this using phasors - see worksheet 4.

The term $\cos \phi$ is known as the **power factor**.

Using phasors, the three types of power can be related in the 'power triangle'.

The **real** power uses the component of the voltage that is in phase with the current, leading to:

$$P = V I \cos \phi$$


The **reactive** power involves the component of voltage that is 90° out of phase with the current and so:

$$Q = V I \sin \phi$$

The **apparent** power is the vector sum of real and reactive power, calculated using $S = V I$.

Power factor can be calculated from the relationship:
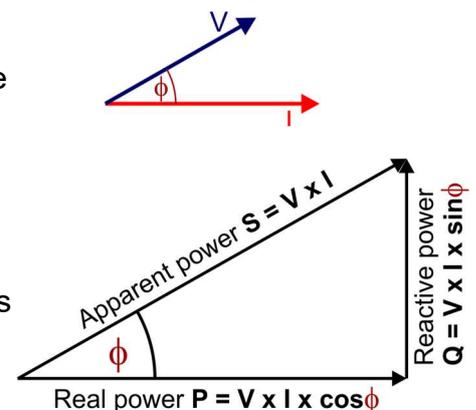
$$\text{Power factor} = \text{real power} / \text{apparent power}$$



Introduction

Introduction to Three-phase Power


Using the hardware continued...

Digital oscilloscope

An oscilloscope ('CRO') monitors signals, usually those that vary over time. It presents the results as a voltage/time graph.

The basic controls on oscilloscopes are:

- Voltage sensitivity - sets the scale on the voltage (vertical) axis;
 - spreads the trace vertically if a lower number is used. The diagram shows a setting of 0.5 V/div.
- Timebase
 - sets the scale on the time (horizontal) axis.
 - spreads the trace horizontally if a lower number is used.
 - The diagram shows a setting of 10 ms/div.
- Trigger
 - sets the threshold signal voltage that starts data-gathering;
 - can be set for either a rising or a falling signal at that voltage level.

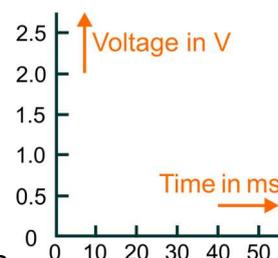


A computer-based oscilloscope, like Picoscope, is a data-logger, that monitors voltages, at regular intervals, and passes the results to software in the computer. There, the data is processed to produce voltage/time graphs, frequency information etc. to be displayed on the monitor, stored as a file, or printed, like other information on the computer.

The Picoscope uses the oscilloscope controls described above, plus:

- AC or DC
 - shows only varying voltages for 'AC' (so centres the trace on 0V;)
 - shows the true voltage levels if DC is chosen.
- Stop / Go
 - **'Stop'** - the trace is 'frozen' (i.e. showing a stored event;)
 - **'Go'** - the trace is showing events in real-time;
 - Click on the appropriate box to change from one to the other.

The settings are selected on-screen using the drop-down boxes provided.

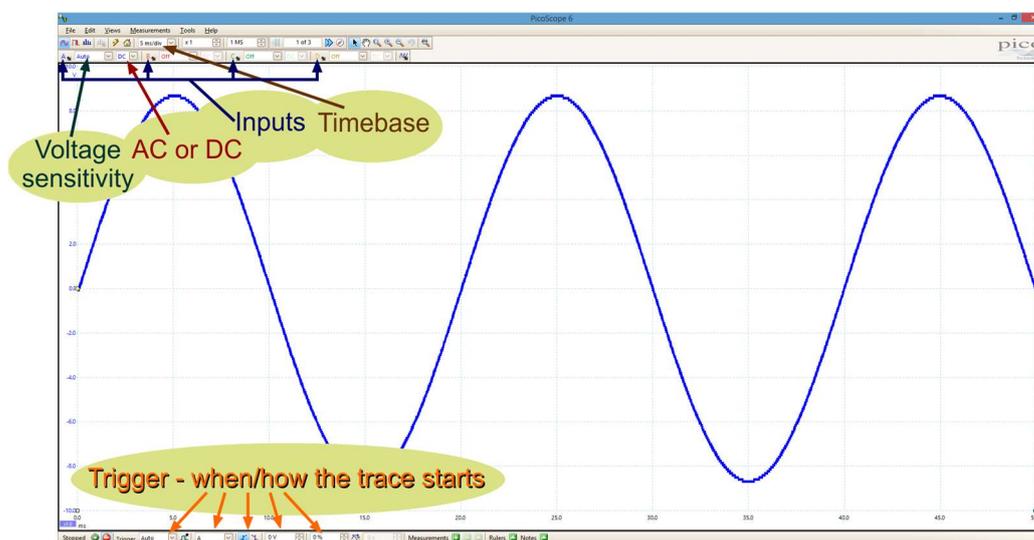The following diagram shows some of the main controls on the Picoscope 6 screen.



Introduction

Introduction to Three-phase Power

Picoscope continued...

In this trace:

Timebase - 5 ms/div

Voltage sensitivity - auto

Trigger - Auto

Ch A

Rising

Threshold - 0 mV

Pre-trigger - 0%

- so the time scale (horizontal axis) is marked off in 5 ms steps.

- so the software adjusts the voltage scale (vertical axis) to suit the signal.

The scale on the left-hand edge of the image increases in 2V steps.

The trace shown has a maximum value of around 8.7V.

- so will show any changes in the signal as they happen.


- so looks at the signal on channel **A** to decide when to start the trace.

- so waits for a **rising** voltage to reach the threshold;

- so starts the trace when the signal on channel **A rises** through **0V**.

- so the display starts with the very first data captured.

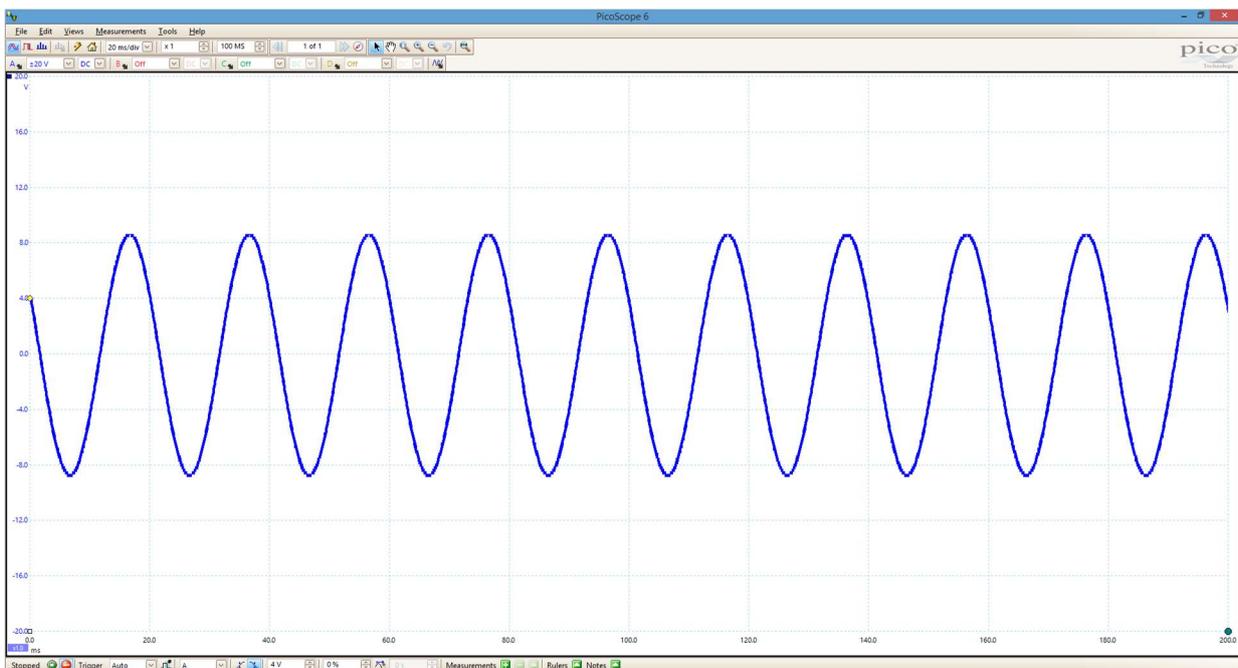For the next trace, the signal is the same, but some of the settings have been changed.



New settings:

Timebase - 20 ms/div

Voltage sensitivity - 4V/div

Trigger - Auto

Ch A

Falling

Threshold - **4V**

Pre-trigger - 0%

- so the time scale is marked off in 20 ms steps.

- so the voltage scale is marked off in 4V steps.

The trace still has a maximum value of around 8.7V.

- so still shows any changes in the signal as they happen.

- so still looks at the signal on channel A to decide when to start the trace.

- so now waits for a **falling** voltage to reach the threshold;

- so starts the trace when the signal on channel A **falls** to **4V**.

- so the display starts with the very first data captured.

More information about using Picoscope is given in the Picoscope User manual, found on the CD-ROM that comes with the instrument or on the website www.picotech.com.

Worksheet 1

Single-phase AC

Introduction to Three-phase Power

'Mains' electricity is traditionally distributed as AC.

The reasons for this include:

- alternators that generate electricity at the power stations are lighter, and cheaper than equivalent DC generators;
- transformers can be used to step the voltage up or down, allowing efficient transmission of electrical power at high voltage (and low current) over large distances.




Over to you:

This worksheet looks at aspects of single-phase AC, using the signal obtained from one output of the three-phase generator, via sockets 'Ph1' and 'N'.

- Build the circuit shown opposite.
- On the three-phase generator:
 - set the frequency to 50Hz;
 - set the amplitude to 6V;
 - switch on.

- Picoscope settings:

Timebase	5ms/div
Channel A	Auto
Channels B, C and D	Off
Trigger	Auto
Threshold	0V
Pre-trigger	0%

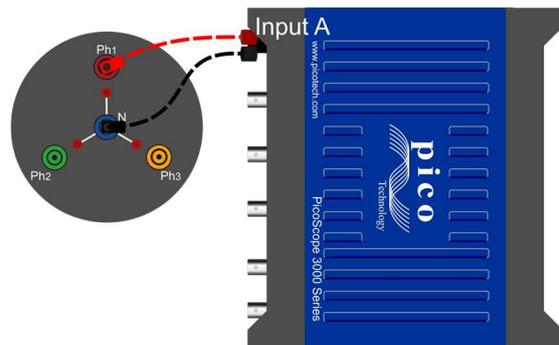

- Obtain a trace showing the AC output and save it for your records.
- Switch off the three-phase generator.
- Now change the settings on the three-phase generator to:
 - frequency 150Hz
 - amplitude 9V.
- Use Picoscope to obtain a new trace.
- Save it for your records, with details of the new settings.

A challenge


Investigate the effect of changing the Picoscope settings.

Worksheet 1

Single-phase AC

Introduction to Three-phase Power

So what?

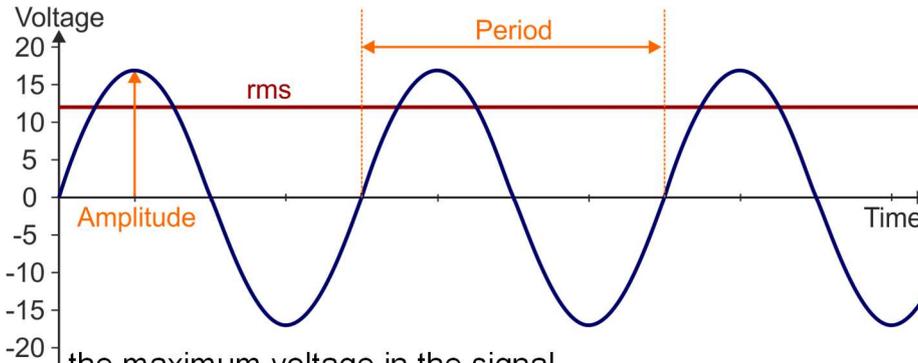

- Amplitude** - the maximum voltage in the signal.
- Period** - the time taken to produce one cycle of the wave, (i.e. 1 peak plus 1 trough)
 - measured in seconds.
- Frequency** - the number of cycles of the wave produced per second;
 - measured in hertz. (1 Hz means one cycle produced every second.)

The relationship between them is:

$$\text{Frequency} = 1 / \text{period}$$

Delivering power:

At times, an AC supply delivers zero volts. At other times, it delivers higher or lower values. A useless fact - the average voltage for an AC supply (any AC supply) is zero!

This certainly does NOT mean that AC supplies do nothing - far from it! - the average power delivered is NOT zero. (For a resistor, R, power delivered = V^2 / R , i.e. depends on voltage squared! Hence, the voltage may be negative but the power delivered is still positive. A negative voltage simply means that the current flows the other way, as you saw in the third circuit.)

For an AC supply, a measure more significant than average voltage is rms voltage. Although it stands for 'root-mean-square' voltage, it is better to think of it as the DC voltage which would deliver the same power to a load.

For a sine-wave signal, peak and rms voltage are linked by:

$$V_{\text{rms}} = 0.7 \times V_{\text{peak}}$$

For your records:

- Copy the diagram of the AC signal, and explain the meaning of the terms *amplitude*, *period* and *frequency*.
- Copy the table and use the measurements you took in the first part of the investigation to complete it.

Amplitude in V	Period in s	Frequency in Hz

- Copy and complete the statement by calculating the rms voltage:
In the first circuit, the rms voltage was

Worksheet 2

Three-phase AC


Introduction to Three-phase Power

Electrical power is transmitted around the country using a three-phase, rather than a single-phase system.

The advantages of three-phase include:

- less copper needed for the transmission cables;
- devices like motors are less affected by vibration - power is delivered more smoothly;
- three-phase alternators are smaller and lighter than equivalent single-phase versions;
- both three-phase and single-phase devices can be powered from a three-phase supply, but the reverse is not true.

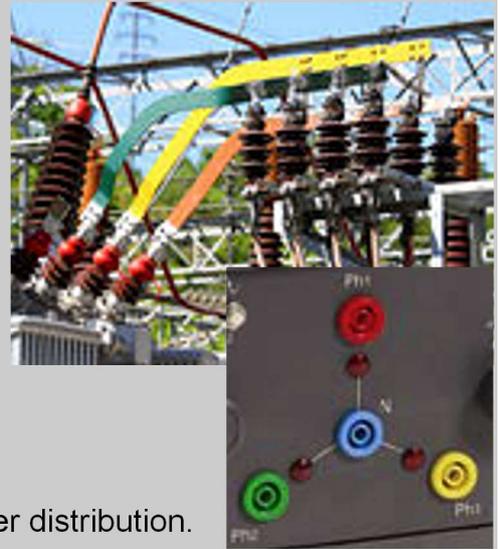This worksheet looks at basic properties of three-phase power distribution.





Over to you:

The two investigations both look at why 'three-phase' is so called - the first at low frequency, using lamps, the second at higher frequency with 'Picoscope'.

- Build the first circuit, using three 12V MES bulbs and holders.
- On the three-phase generator, set the frequency to 0.1Hz (fixed), and the amplitude to 6V.
- Switch it on and observe the lamps. They are neither in step, nor completely out of step, but reach maximum brightness at different times.

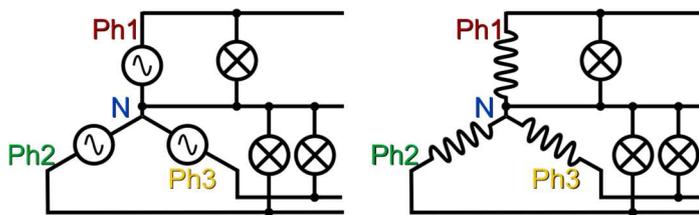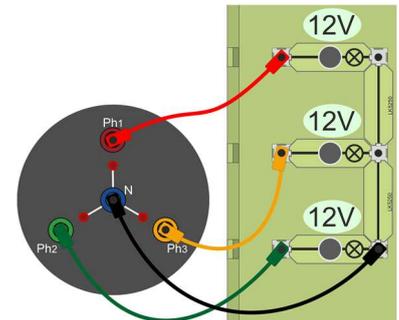The diagram that follows shows two ways to represent this circuit, using different symbols for the three-phase generator.




Ⓢ = AC generator
 ⚡ = generator winding (coil)

- Build the second circuit, connecting the three-phase generator to Picoscope, as shown.

Again, notice the ground clip connecting Picoscope ground to terminal 'N'.

Picoscope settings:

Timebase	5ms/div
Channel A, B and C	Auto
Trigger	Auto
Threshold	0V
Pre-trigger	0%

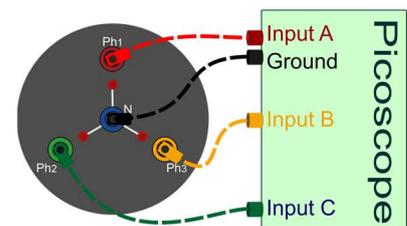

- Set the generator frequency to 50Hz, and amplitude to 6V and switch it on.
- Obtain a trace showing the three outputs and save it for your records.

Worksheet 2


Three-phase AC

Introduction to Three-phase Power

So what?


The diagram opposite shows typical output from the Picoscope.

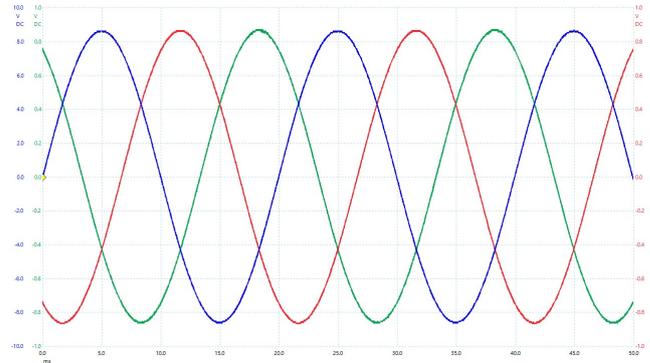Each phase, shown in different colours, has the same time period, 20ms. They peak at times separated by $20/3 = 6\frac{2}{3}$ ms.



Phase angle:

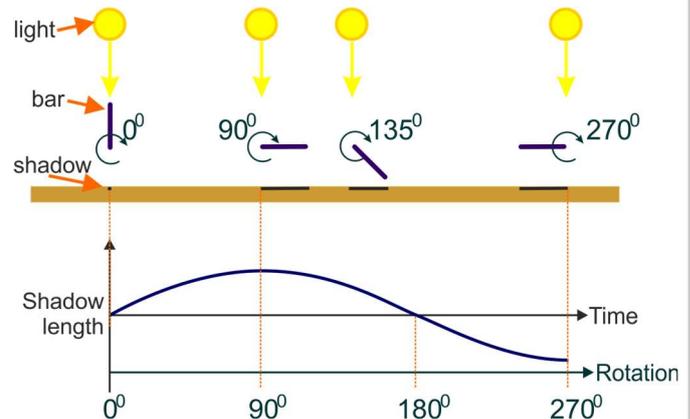Imagine a bar rotating around one end. Above it, a light shines down, creating a shadow of the bar. As the bar rotates, the shadow gets longer, then shorter, then zero, then longer in the other direction, and so on.




As the bar continues to rotate, the shadow sequence repeats. One complete rotation of the bar creates one cycle of the sequence.

We can use the same idea to describe phase in alternating voltage signals. Here, the starting point and end point of one cycle of the signal are separated by a phase difference of 360° .

Using the information given above, one cycle of each phase lasts 20ms, so points which are 20ms apart have a phase angle of 360° between them.

The peaks of the three phases are separated by 6.66ms.

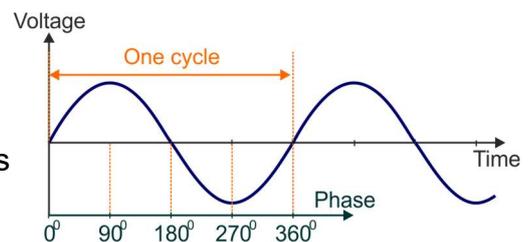In other words, the phases are separated by phase angles of $(360/20) \times 6\frac{2}{3} = 120^\circ$.



For your records:

- Describe five advantages of three-phase over single-phase power transmission. (You may need to carry out a little research on this, using the internet, for example.)
- Draw two cycles of a sine wave signal. Add a second signal where the phase angle between them is 180° .
- Do the same again, with a phase angle of 270° between the two signals.

Worksheet 3


More phase basics

Introduction to Three-phase Power

It's complicated!

The voltages and currents change in size, and direction over time. There appear to be three separate sources, all peaking at different times.

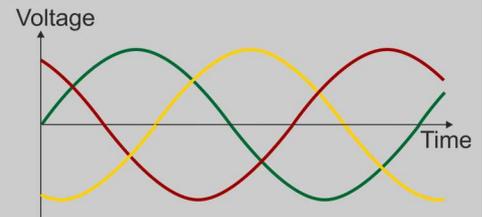
We need a word to describe all of this - phase.



Over to you:

These investigations focus on the relationship between current and voltage in three different types of load - resistive, capacitive and inductive. The inductive load is created by joining the coils of the three-phase motor in series.

- Build the circuit shown opposite.
This time we are monitoring the AC voltage across the 10Ω resistor and the current flowing through it.
- Clamp the jaws of the current clamp around one of the wires from the three-phase generator.
- Use the same settings for the timebase, for channel A and for the trigger. Switch channel B to 'Auto'.
- Switch on the current clamp, on the 20A range.
- **Check that the three-phase generator is set to the '6V' output or the 10Ω resistor may overheat!**
Switch on the generator.
- Obtain a trace comparing the AC voltage across the resistor with the current flowing through it, and save it for your records.
- Notice that the two AC signals (the voltage across the resistor and the current through it), are in step (in phase,) with each other.
- Switch off the three-phase generator and the current clamp.

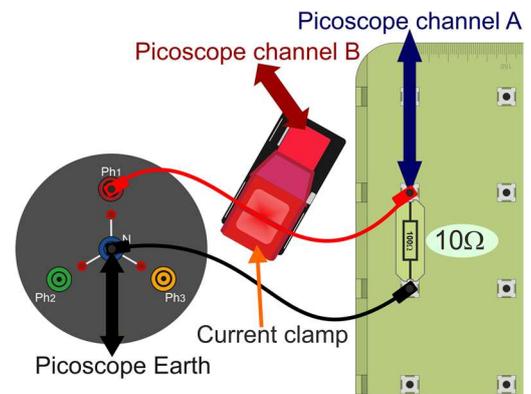

A challenge:

Using the same approach, modify the circuit to obtain voltage and current traces for:

- a $33\mu\text{F}$ capacitor;
- an inductor, made by using one of the motor coils.

Worksheet 3

More phase basics

Introduction to Three-phase Power

So what?

A typical Picoscope trace for the resistor is shown opposite.

The red trace indicates the current flowing through the resistor and the blue trace the voltage across it. They rise and fall in step. They are in phase.

When you modified the circuit to investigate the other components, you should have obtained traces like the ones shown opposite.

- In the capacitor, current reaches peak value when the voltage is zero!
- In the inductor, the voltage peaks when the current is zero.

Phase angle:

Using phase angles, we can refine our earlier statements:



- In a capacitor, the current signal leads the voltage signal by a phase angle of 90° .
- In the inductor, voltage leads current by a phase angle of 90° .

Phase voltage vs line voltage:

In discussing three-phase systems, two different measures of voltage are used - phase voltage and line voltage.

- Phase voltage - measured between a phase terminal and the common ('N') terminal.
- Line voltage - measured between one phase and another.

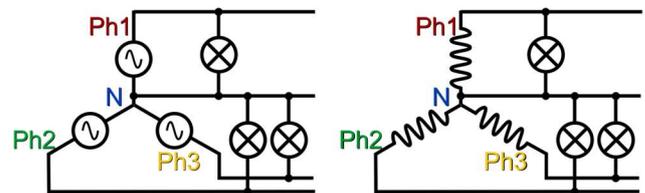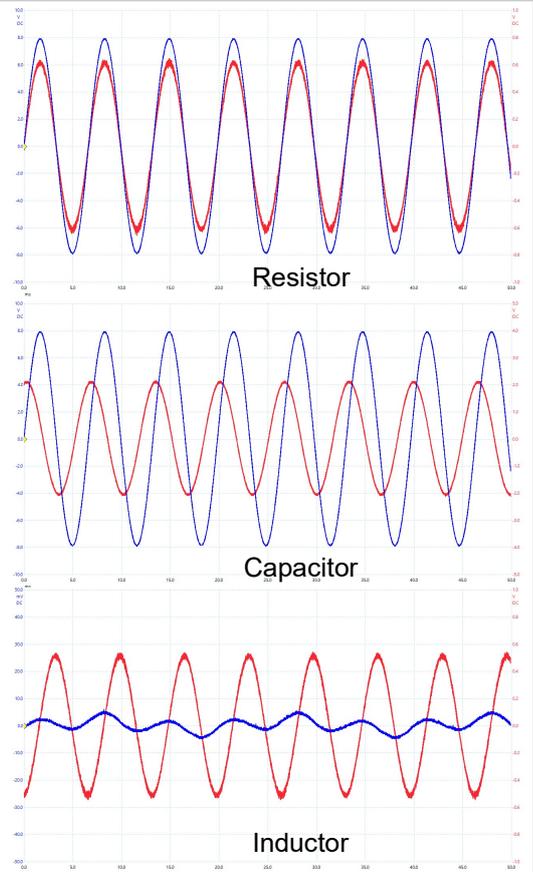The circuit you set up earlier measured phase voltages.



For your records:

- Copy the diagram showing the difference between phase and line voltage.
- Copy and complete the statement:
For a resistive load, AC voltage and current are
- What is the phase angle between current and voltage in a resistor?
- Copy the two bullet points describing phase angles in capacitors and inductors.

Worksheet 4

And now the phasor

Introduction to Three-phase Power

It is even more complicated than we made out!

We saw that the current flowing through the component may not be in phase with the voltage across it. What's worse, the size and direction of both change over time!

The language of AC is now extended, bringing in the phasor, (not the 'phaser' - that belongs in 'Star Trek'!)


The worksheet begins by using the three-phase motor, on a three-phase supply and then on a single phase and then turns to phasors and their interpretation.



Over to you:

Three-phase supply:

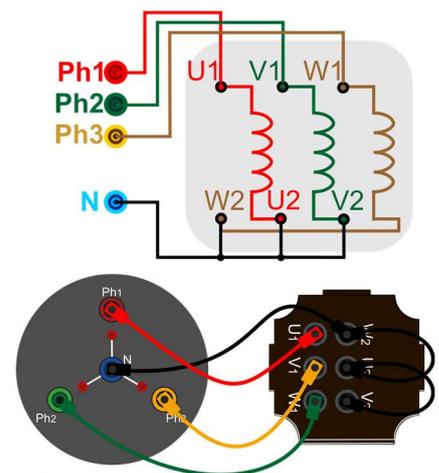- Build the first circuit, shown opposite.
- Set the frequency to 0.1Hz and the amplitude to 6V.
- Switch on the three-phase supply.
- Carefully rest one finger on the motor flywheel, to judge how smoothly the torque is applied.
- What is the effect of turning the amplitude to 9V?
- What is the effect of increasing the frequency to 50Hz?
- What happens when you increase the frequency to 150Hz?




Challenges:

Investigate what happens when you change to phase connections to the motor, or leave one disconnected? Can you reverse the direction of rotation?

Single-phase supply:

- Build the second circuit, shown opposite. It uses only one phase of the power supply to drive two sets of coils, the 'U' and 'V' coils, (if set up as in the diagram). The capacitor adds a phase shift between the supplies to the two coils.
- Using the same frequency and amplitude of 6V, switch on.
- When the motor is running, disconnect one of the capacitor leads. It should continue running.
- Again, rest a finger on the motor flywheel, to judge how smoothly the torque is applied.
- Does the motor need the second coil, or will it run using just the supply to one coil?
(Test by disconnecting one of the capacitor leads.)
- Investigate the effects of changing the frequency and amplitude of the supply, with and without the capacitor connected.

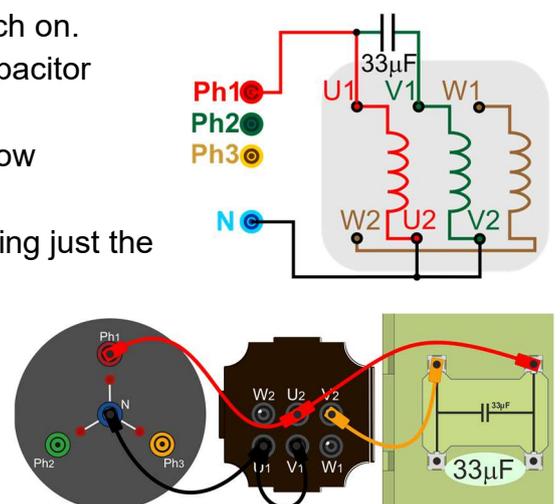

Worksheet 3

And now the phasor

Introduction to Three-phase Power

So what?


To understand AC circuits containing capacitors and inductors, you will need to understand phasors. The first step is to look at vectors:

Vectors - vector quantities, like forces and velocities, are described fully only when both size and direction are given. Combining them together is not straightforward!

For example, the diagram shows two tugs pulling a ship. The force exerted by each tug is shown as an arrow.

- its length represents the size of the force;
- its direction is the direction of the force.

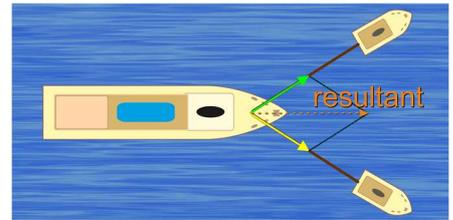To find the total (**resultant**) force, complete the parallelogram and construct the diagonal, as shown. Its length gives the size of the resultant force, its direction, the direction of the resulting force.



Phasors - Current and voltage have size and direction, like vectors, but these change with time! They can also be represented by arrows, but these rotate!


The length of the horizontal component gives the size of the voltage or current at that instant. As the phasor rotates, this increases to a maximum, decreases to zero, increases and so on, (like the rotating bar in worksheet 2.)

Direction - when the horizontal component is on the right-hand side of the diagram, current flows to the right, say, and when the component is on the left-hand side, it flows to the left.


Combining phasors - also uses the parallelogram rule, but the current is being 'pulled' by a number of voltages!

For example, in the circuit described by the diagram opposite:

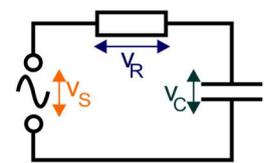- the supply voltage, V_S , is split between the resistor and capacitor;
- the current through both is the same as they are in series;
- current is in phase with resistor voltage, V_R , but leads capacitor voltage, V_C , by 90° .



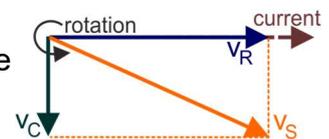This leads to the phasor diagram opposite. (The lengths for V_R and V_C are arbitrary.) Although all phasors are rotating, (at the supply frequency,) the diagram shows the situation when current is maximum.



- Check the diagram to make sure that you can see the information about V_R , V_C and current. The vector parallelogram rule gives V_S as the resultant of V_R and V_C .

For your records:

- Describe how a current phasor contains information about its size and direction.
- Copy the circuit diagram and phasor diagram given above. Explain the link between them.
- A pure inductor (no resistance) is added in series with the resistor and capacitor. Draw the circuit diagram and phasor diagram for the new circuit. Choose equal sizes for V_C and V_L .
(When added together, they cancel each other out!)

Worksheet 5


It's a star!

Introduction to Three-phase Power

There are two ways to connect up three-phase supplies and loads - the star, (or 'Wye', because of its resemblance to the letter 'Y') and the delta configurations.

The diagram shows a star-connected three-phase supply driving a star-configured load.

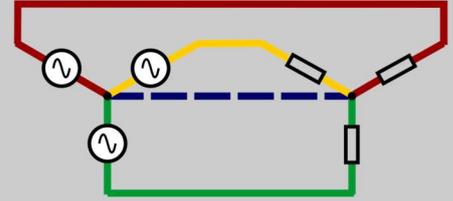In the star configuration, there is a 'neutral' point, where all phases, or loads are connected together.



Over to you:

- Build the circuit shown opposite.
- On the three-phase generator, set the frequency to 50Hz and the amplitude to 6V and switch on.


Voltages in a star configuration:

Phase voltages:

- Use a multimeter on the 20VAC range to measure the 'red' phase voltage, V_R , across the top resistor.
- Similarly, measure 'yellow' phase voltage, V_Y , across the middle resistor and 'green' phase voltage, V_B , across the bottom one.
- Enter all values into the table.

Line voltages:

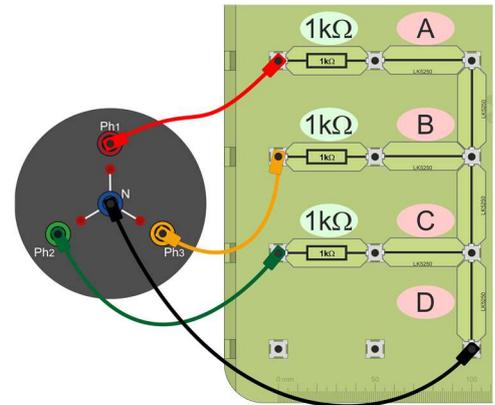- With the same settings, measure the line voltage, V_{RY} , between the 'red' phase and the 'yellow' phase.
- Similarly, measure the line voltages V_{RG} and V_{YG} .
- Enter all values into the table.



Voltage	Value in V
'Red' phase voltage, V_R	
'Yellow' phase voltage, V_Y	
'Green' phase voltage, V_G	
line voltage V_{RY}	
line voltage V_{RG}	
line voltage V_{YG}	

Currents in a star configuration:

- Remove connecting link A. With a multimeter on 20mA AC, measure the phase current I_R , and enter the result in the table.
- Replace connecting link A.
- In the same way, measure phase currents I_Y and I_G . Enter their values in the table.
- Remove connecting link D. Measure the current in the neutral wire, I_N and enter its value in the table.

Current	Value in mA
'Red' phase current, I_R	
'Yellow' phase current, I_Y	
'Green' phase current, I_G	
Neutral current, I_N	

Worksheet 5

It's a star!

Introduction to Three-phase Power

So what?

Phase voltages - The magnitudes of the three phase voltages are virtually identical. This is because of the way the three-phase generator is constructed.

Line voltages - Theory predicts the relationship:

$$\text{Line voltage} = \sqrt{3} \times \text{Phase voltage}$$

- Complete the table, using your measurements from the previous page.

Voltage	Value in V	$\sqrt{3}$ x phase voltage
'Red' phase voltage, V_R		
'Yellow' phase voltage, V_Y		
'Blue' phase voltage, V_B		
line voltage V_{RY}		
line voltage V_{YB}		
line voltage V_{BR}		

- Do the results support this relationship?

Current in a star configuration -

This circuit has the three-phase power source connected in a star, and the loads connected in a star. The neutral points in each star are connected together. In this case, the load is known as a **balanced load**, as the impedance (in this case resistance) in each phase is identical ($1\text{k}\Omega$).

- As can be seen from the circuit, phase current and line current are identical.
- Notice that the currents in the three phases are identical - not surprising, as the phase voltages are identical and the loads are identical.
- What may be a surprise is the value of current in the neutral wire - virtually zero!

This is the result of the phase differences between the currents.

- They are not in phase.
- They do not all reach maxima together.
- They do not add together arithmetically.

A challenge - Remove the neutral wire. Does it make any difference to your readings?

Investigate what happens when the load is unbalanced. (Swap one of the $1\text{k}\Omega$ resistors for a different value, such as $2.2\text{k}\Omega$.)

For your records:

- Draw the circuit diagram for the system you built for this investigation.
- Summarise the findings given in the previous section.
- Explain the mystery of the 'missing current' when a balanced load was used. Where has it gone?
- Explain why electricity is usually transmitted using a four-wire system, rather than a three-wire system.

Worksheet 6


On the delta

Introduction to Three-phase Power

The other way to configure three-phase circuits is to use the 'delta' connection, (so-called because of the similarity of the shape to the Greek letter 'delta' (Δ)).



The diagram shows a three-phase power source, connected in delta configuration to a load, also in delta configuration.

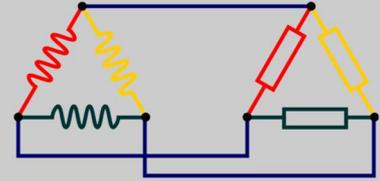This time, there is no neutral point, and only three wires link the power source and load.



Over to you:

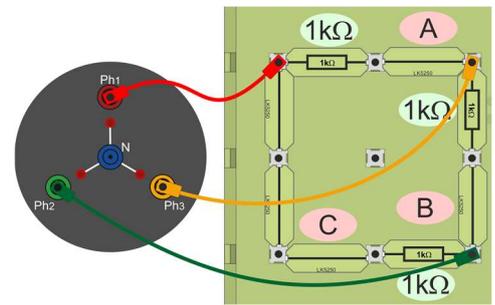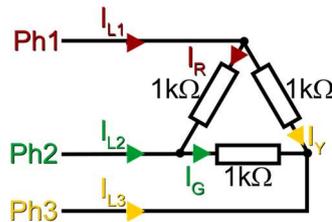- Build the circuit shown opposite. The delta connection may not be immediately obvious. Compare it with the circuit diagram that follows:
 - phases are connected together through $1k\Omega$ loads;
 - the three load resistors are connected in a loop.



- On the generator, set the frequency to 50Hz and the amplitude to 6V and switch on.

Voltages in a delta configuration:

As can be seen from the diagram, phase voltage and line voltage are now identical.

- Use a multimeter to measure the line voltages across the three $1k\Omega$ loads.
- Record them in the table.

Line voltage	Value in V
V_{12}	
V_{13}	
V_{23}	

Currents in a star configuration:

- Remove connecting link A. With the multimeter on the 20mA AC range, measure the phase current, I_R , through the $1k\Omega$ resistor connected between phases **Ph1** and **Ph2**.
- Enter the result in the table.
- Replace connecting link A.
- Next, measure phase currents I_Y and I_G .
- Enter their values in the table.
- Remove the red wire connecting **Ph1** to the load.
- Replace it with the multimeter and read line current I_{L1} . Enter its value in the table.
- Do the same for the other two line currents, I_{L2} and I_{L3} .

Current	Value in mA
phase current, I_R	
phase current, I_Y	
phase current, I_G	
line current I_{L1}	
line current I_{L2}	
line current I_{L3}	

Worksheet 6

On the delta

Introduction to Three-phase Power

So what?

Theory predicts the relationship:

$$\text{Line current} = \sqrt{3} \times \text{Phase current}$$

- Complete the table, using your measurements from the previous page.

Current	Value in mA	$\sqrt{3} \times \text{phase current}$
phase current, I_R		
phase current, I_Y		
phase current, I_G		
line current I_{L1}		
line current I_{L2}		
line current I_{L3}		

- Does it relationship?

support this

Summary:

In a delta configuration:

Line voltage = Phase voltage

Line current = $\sqrt{3} \times \text{Phase current}$

A challenge -

- Connect the three-phase motor using a delta configuration:
 - connect the three coils in delta formation - U2 to V1, V2 to W1 and W2 to U1.
 - connect the three phases to U1, V1 and W1.
- What happens when you reverse two of the phases?
- Compare the performance of the motor in delta configuration with that seen earlier using the star configuration.

For your records:

- Copy the circuit diagram showing a delta-configured three-phase supply, driving a delta-configured three-phase load.
- Summarise the findings of this investigation.
- Using an internet search engine, or text books, draw up a table of relative advantages and disadvantages for star and delta configurations.
- Draw the circuit diagram for the delta-configured motor on the three-phase supply.
- Compare the performance of the motor when in star and in delta configuration.

Worksheet 7

Half-wave rectification

Introduction to Three-phase Power

Some electrical devices require a DC supply and will not run on AC.

Rectification is the process of turning an AC supply into DC. It relies on the fact that diodes allow appreciable current to flow in one direction only.

Comparing rectified three-phase to single-phase:


The advantage:

- the result is much smoother.

The disadvantage:

- it requires more diodes to accomplish it.

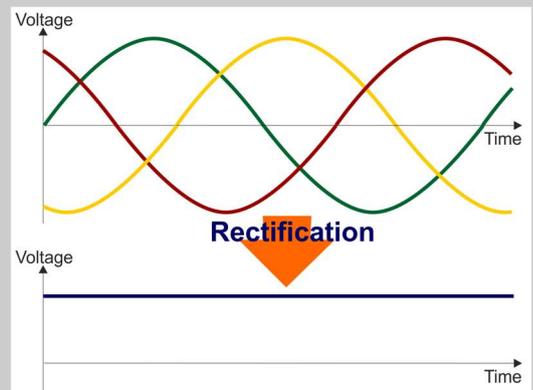This worksheet introduces the process by looking at half-wave rectification.




Over to you:

- Build the circuit shown opposite. (The circuit diagram is given underneath it.)
It uses the three-phase generator, in star configuration, to drive current through a $1\text{k}\Omega$ load. Each phase has a diode in series to ensure that current flows only one way through the load.


Notice the Picoscope ground clip!

- On the three-phase generator, set :
 - the frequency to 50Hz;
 - the amplitude to 9V.
- Use the following Picoscope settings:

Timebase	5ms/div
Channel A, B, C and D	Auto
Trigger	Auto
Threshold	0V
Pre-trigger	0%

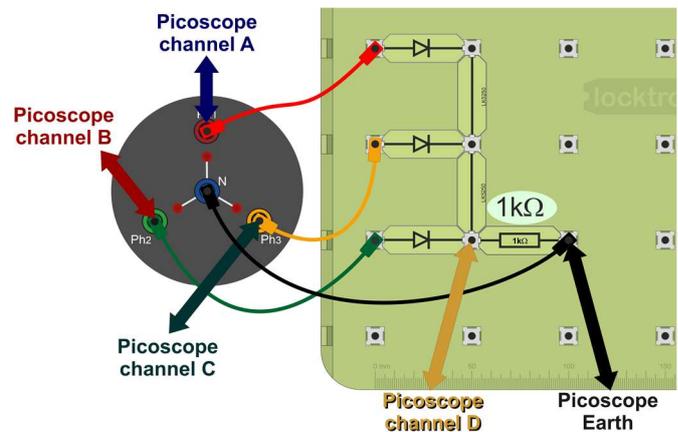

- Switch on the three-phase generator.
- Obtain a trace showing the three phases delivering power to the load and the half-wave rectified output applied to it.
- Save it for your records.
- To make it clearer what is happening, turn off channels B and C on Picoscope and obtain another trace, showing the outputs on channels A and D, i.e. one input phase and the output.
- Save it for your records with an explanation of what it shows.

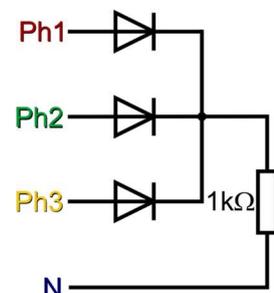


Worksheet 7

Half-wave rectification

Introduction to Three-phase Power


So what?

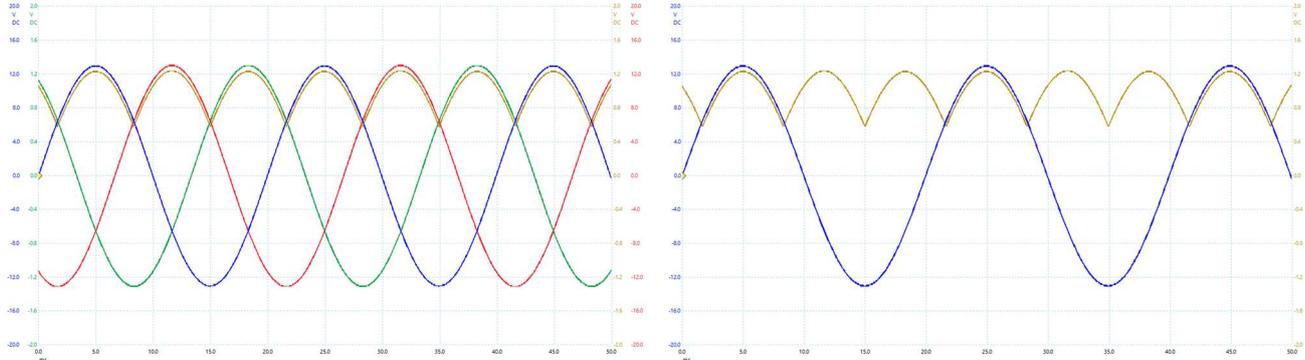The diagrams show typical signals. The rectified output is on channel D, shown in gold.



Notice that it sits below the corresponding AC phase signal. This is because of the 0.7V (approx.) drop across a conducting silicon diode. The trace is always positive, and so it is a DC signal, though not smooth DC.

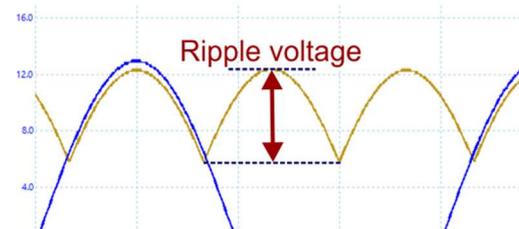In one AC cycle, there are three peaks in the rectified signal, one for each of the three phases. This indicates that it is half-wave rectification only - the negative half-cycle of each phase is ignored. (Compare this with the next worksheet!)



The variation in the output voltage, (across the load,) is known as the ripple voltage.

Challenges -


- Connect a 33 μ F non-electrolytic capacitor in parallel with the 1k Ω load.
- Obtain new Picoscope traces to see the effect on the ripple voltage.

A typical output is shown opposite.

Notice the reduced ripple!

- What is the effect on ripple voltage of using different values of load resistor?

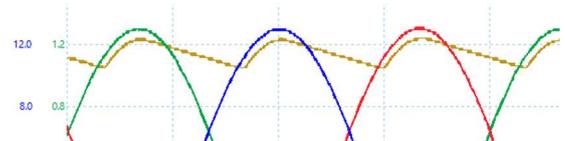You could increase the load resistance by connecting several 1k Ω resistors in series, or reduce it by connecting them in parallel. (Two 1k Ω resistors in parallel have a combined resistance of 0.5k Ω , four in parallel have a combined resistance of 0.25k Ω .)



For your records:

- Draw the circuit diagram for a three-phase half-wave rectifier, and include capacitor smoothing.
- Explain why the output of this circuit is considered to be DC.
- Explain the term 'ripple voltage' and explain why adding a smoothing (or 'reservoir',) capacitor reduces the ripple.

Worksheet 8

Full-wave rectification

Introduction to Three-phase Power

A common use of rectification is in motor vehicles. These generate three-phase electricity using alternators, which are smaller and lighter than equivalent DC generators.

The majority of the vehicle's electrical system requires a DC supply, and so, built into the alternator is a full-wave rectifier.

The previous worksheet looked at half-wave rectification, leading to a DC output voltage, but with a ripple voltage.

This is often undesirable, as it can cause audible 'hum' in audio equipment and spurious effects in digital systems.

Full-wave rectification reduces this ripple voltage, at the cost of additional components.



Over to you:

- Build the circuit shown opposite. Notice the Picoscope ground clip! Make sure that all diodes are connected the right way round!


Without specialised probes, you can not obtain traces of all phases AND the full-wave output simultaneously - that would short-circuit part of the circuit. Instead, use only one probe to monitor the output across the load, as shown.

Picoscope settings:

Timebase	5ms/div
Channel A	Auto
Channels B, C and D	Off
Trigger	Auto
Threshold	0V
Pre-trigger	0%

- Set the three-phase generator frequency to 50Hz and amplitude to 9V.
- Switch it on.
- Obtain a trace showing the output across the 1kΩ load.
- Save it for your records with an explanation of what it shows.
- Connect a 33μF capacitor in parallel with the 1kΩ load and repeat the process.

(To see the relationship between the output and phases, move the Picoscope channel A probe to examine each phase in turn.)

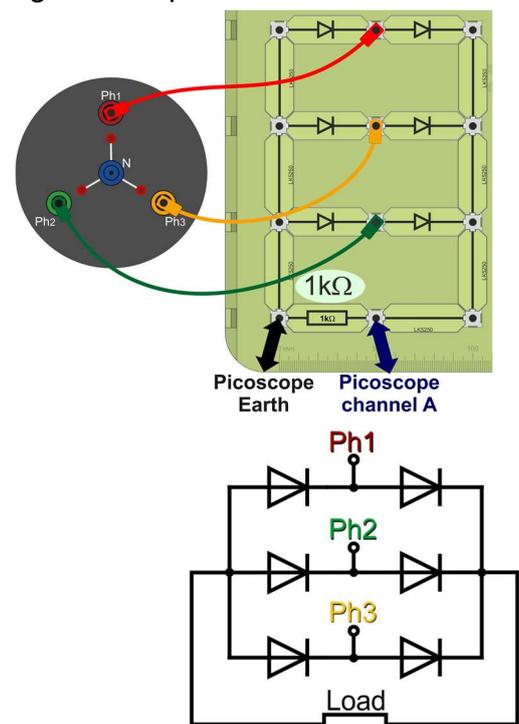

Worksheet 8

Full-wave rectification


Introduction to Three-phase Power

So what?

The two traces opposite show typical Picoscope results, without (top trace) and with smoothing (bottom trace).

Compare them with those obtained for half-wave rectification.

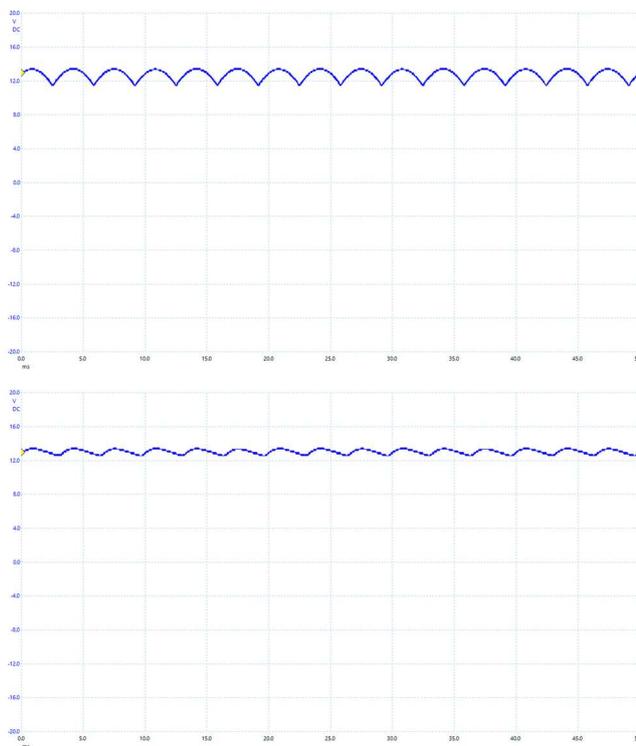The amplitude of the ripple voltage is much smaller and the frequency is higher than with half-wave rectification.



A challenge -

As in the previous worksheet, investigate the effect of load resistor size on ripple voltage.

For your records:

- Draw the circuit diagram for a three-phase full-wave rectifier, including capacitor smoothing.
- In investigating this circuit:
 - what indicated that the output was DC?
 - what indicated that it was a full-wave rectified output, as opposed to half-wave?
- Describe *and explain* the effect on ripple voltage of increasing the size of:
 - the load resistor
 - the smoothing capacitor.

Worksheet 9

Delivering power

Introduction to Three-phase Power

In the end it is a matter of delivering power from transmitter to load. Not surprisingly, there is a complication! Real power is the product of voltage and current *in phase with the voltage*. As we have seen, for many loads, current and voltage are not in phase.


This worksheet examines how this situation is handled, in three circuits. Two use a single phase supply in circuits which contain reactance. The third uses a three-phase supply to drive the three-phase motor.



Over to you:


An R-C circuit:

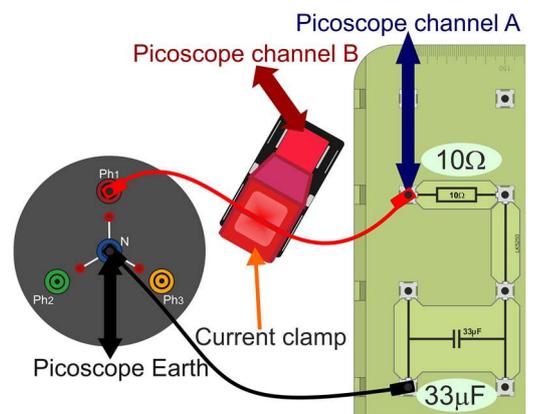- Build the top circuit shown opposite .
- Set the three-phase generator frequency to 150Hz and amplitude to 6V. Switch it on.
- Use the same Picoscope settings as in the previous worksheet.
- Obtain and save a trace showing the supply voltage and current through the circuit.
- Switch off the generator and the current clamp.




An R-L circuit:

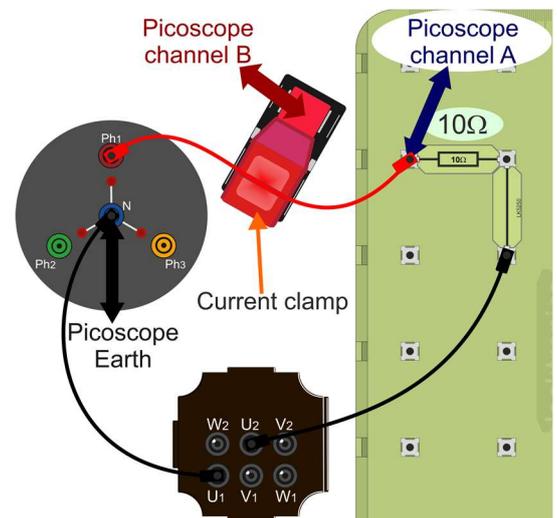- Build the middle circuit.
- Use the same settings as before for the three-phase generator and for the Picoscope.
- Switch on the generator.
- Obtain and save a trace showing supply voltage and current through this circuit.
- Switch off the generator and the current clamp.



The three-phase motor:

- Build the bottom circuit.
- Once more, use the same settings for the three-phase generator and for the Picoscope.
- Switch on the generator.
- Obtain and save a trace showing supply voltage and current through one phase of this circuit.
- Switch off the generator and the current clamp.

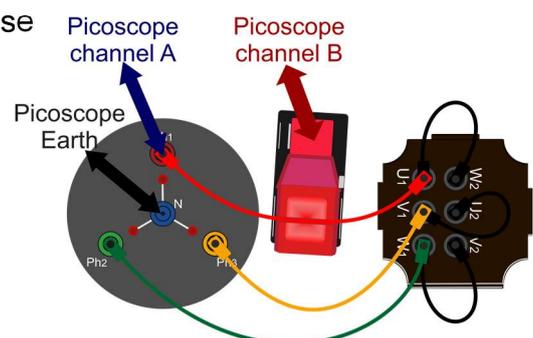

Worksheet 9


Delivering power

Introduction to Three-phase Power

So what?

The traces produced in the three circuits can be analysed to extract the real power delivered to the load devices. The procedure is outlined below, using a section of a current/voltage trace obtained for a R-L circuit to extract phase angle ϕ .

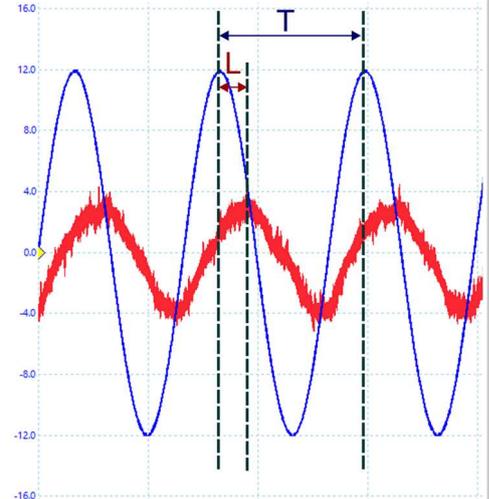The applied voltage is shown by the blue trace, current by the red. The amplitude of the current trace is small and affected by electrical noise. Voltage leads current, as we expect in a circuit containing inductance.



- Draw vertical lines through two adjacent voltage peaks and a current peak, as shown.
- Use the time scale to measure times **T** and **L**.
T is the period of the signal.
L is the time lag experienced by the current.
 Sample results are: **T** = 6.7ms **L** = 1.3ms

- **T** is the time between points with a phase angle of 360° between them. Hence, 1.3ms represents a phase difference of $(1.3 / 6.7) \times 360^\circ$ or 70° approximately
In this R-L circuit, voltage leads current by a phase angle of around 70° . This implies a phase factor of 0.34 (i.e. $\cos 70^\circ$).

- From the traces,
 peak voltage = 12.0V giving $V_{\text{rms}} = 8.4\text{V}$.
 peak current reading = 7mV.
 With the current clamp on the 20A (i.e. 1mV/10mA) range,
 peak current is $7 \times 10 = 70\text{mA}$, giving $I_{\text{rms}} = 49\text{mA}$.

Putting all this together:

$$\begin{aligned} \text{Real power delivered to the system, } P &= V_{\text{rms}} I_{\text{rms}} \cos \phi \\ &= 8.4 \times 49 \times 10^{-3} \times 0.34 \\ &= \mathbf{0.14W} \end{aligned}$$

$$\begin{aligned} \text{Apparent power, } S &= V_{\text{rms}} I_{\text{rms}} \\ &= \mathbf{0.41VA} \end{aligned}$$

For your records:

- In the same way, determine the real and apparent power for the R-C and R-L circuits you set up in this investigation.
- The three-phase motor is a balanced load.

The total power delivered = 3 x power delivered to one phase.

Use your results from the third circuit to determine the real power delivered to the motor.

Worksheet 10

Power factor correction

Introduction to Three-phase Power



A low power factor means that more current is needed to transfer a given quantity of useful energy.

The extra current stores energy, temporarily, in the magnetic field of a motor for example. It then returns to the power supply a short time later.


It delivers the same useful power but thicker cables, heavier transformers etc. may be needed to cope with the extra current and the consumer may incur extra charges as a result.

Over to you:

A resistive load:

The three lamps represent a purely resistive load.

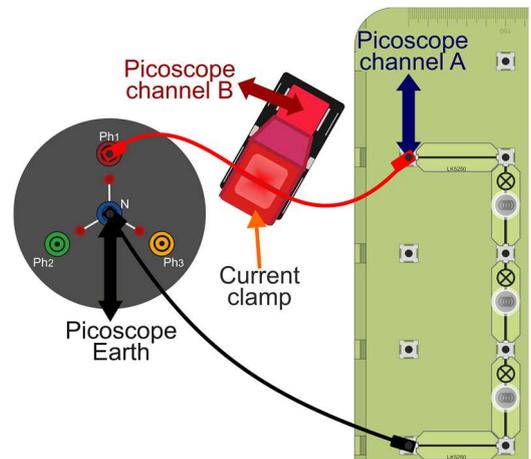
- Build the circuit shown opposite .
- Set the three-phase generator frequency to 150Hz and amplitude to 6V. Switch it on.
- Use the same Picoscope settings as in worksheet 8.
- Obtain and save a trace showing the supply voltage and current through the circuit.
- Switch off the generator and the current clamp.



An inductive load:

One coil of the motor is used as an inductive load.

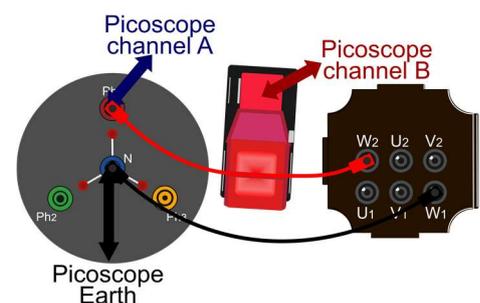
- Build the second circuit.
- Use the same generator and Picoscope settings.
- Switch on the generator.
- Obtain and save a trace showing the supply voltage and current through this circuit.
- Switch off the generator and the current clamp.



An inductive load with power factor correction:

A capacitor balances the inductive reactance of the load.

- Build the third circuit.
- Use the same generator and Picoscope settings.
- Switch on the generator.
- Obtain and save a trace showing the supply voltage and current through the circuit.
- Switch off the generator and the current clamp.

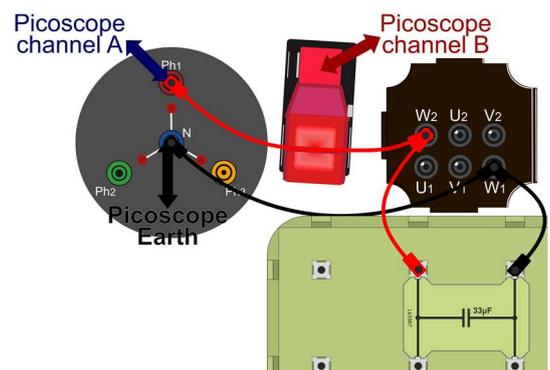

Worksheet 10

Power factor correction

Introduction to Three-phase Power

So what?

With a resistive load, current is in phase with voltage, the optimum arrangement for efficient power delivery.

For the uncorrected inductive load, however, that is not the case. In inductors, current lags behind voltage.

The coloured area shows the time over which power is delivered to the load. As this is a relatively short period, the current must be large to deliver enough energy.

The aim of power factor correction is to bring current and voltage back into phase - extending the time over which power is delivered. The current needed to deliver the required energy can then be smaller.

In reality, most loads are resistive or inductive overall.

Here are some examples:

- resistive - incandescent lamp, heater;
- inductive - motors, relays, transformers.

Inductive loads use added capacitors for power factor correction.

For a motor, the value of capacitor needed to do this depends on aspects like the speed of the motor, its load and the frequency of the supply. This causes complications when there are a number of motors on the same power supply and when their speed and loads vary.


Some industrial sites use banks of capacitors to move the overall power factor back towards a value of unity in order to reduce electricity costs.

The benefits of power factor correction:

- reduced electricity charges and no financial penalty from the electricity supplier;
- reduced heat losses in cables, switchgear, transformers and distribution equipment;
- prolonged life of transmission and generation equipment;
- reduced voltage drop in cables, allowing the use of smaller gauge cables.

A challenge:

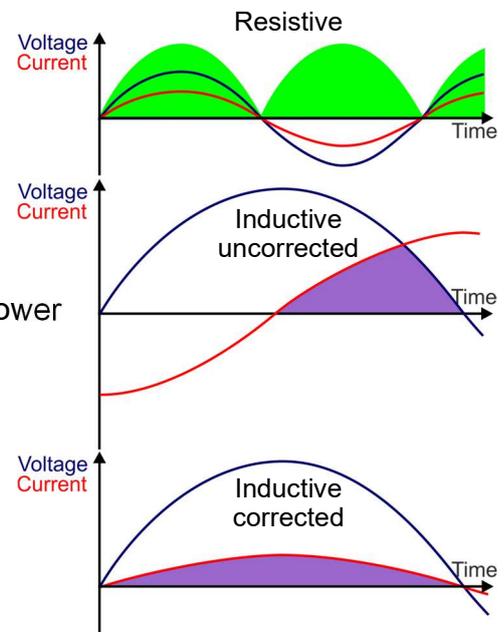Investigate the effect of changing the frequency of the three-phase supply. What frequency gives the best power factor correction for the inductive load?



For your records:

- Explain, using voltage / time graphs, the meaning of the term 'power factor correction'.
- Describe two advantages of power factor correction to an industrial consumer.
- Draw the circuit diagram for circuit that uses a single-phase AC supply to drive an electric motor and incorporates power factor correction.

Instructor Guide

Introduction to Three-phase Power

About this course

Introduction

The course is essentially a practical one. Locktronics equipment makes it simple to construct and test electrical circuits. The end result mirrors the circuit diagram, thanks to the circuit symbols printed on the component carriers.

Aim

The course introduces students to concepts used in three-phase electrical transmission and utilisation. These form the basis for a deeper study of this topic.

Prior Knowledge

It is recommended that students have followed the 'Electricity Matters 1' and 'Electricity Matters 2' or have equivalent knowledge, covering basic electrical concepts - current, voltage, resistance and the construction and testing of circuits, using a range of measuring instruments, including multimeters and oscilloscopes.

Learning Objectives

On successful completion of this course the student will be able to:

- explain the meaning of the terms 'amplitude', 'period' and 'frequency' in the context of AC electrical signals;
- state and use the relationship between 'period' and 'frequency';
- recognise and use the units for these quantities;
- measure these quantities given a sinusoidal waveform of a signal;
- distinguish between peak and r.m.s. values for a sinusoidal electrical signal, and use the formula that relates them;
- use a digital oscilloscope, such as Picoscope, to obtain voltage/time graphs of AC electrical signals;
- draw a circuit diagram showing a three-phase power source;
- describe five advantages of three-phase power supplies over single-phase supplies;
- explain the term 'phase angle' and justify that the phase angle between the three phases in the supply is 120° ;
- draw two sinusoidal signals separated by a given phase angle;
- use a current clamp to obtain a current/time graph of AC electrical signals;
- state the phase relationships between current and voltage in resistors, inductors and capacitors;
- distinguish between the terms 'phase voltage' and 'line voltage' in a three-phase system;
- drive a three-phase motor from a single phase source, using a capacitor to create a phase shift;
- extract magnitude and direction for a vector quantity from the vector;
- combine together two vector quantities using the parallelogram construction to obtain the resultant;
- distinguish between vector and phasor quantities;
- draw a phasor diagram to show the relationship between currents and voltages in a series LCR circuit;
- connect three resistors in star configuration;
- distinguish between a balanced load and an unbalanced load in a three-phase system;
- explain why the neutral (return) wire is unnecessary in a balanced load three-phase system;
- explain why the neutral (return) wire is normally used in a three-phase transmission system;
- connect three resistors in delta configuration;
- state and use the relationship between phase voltage and line voltage in star and delta configurations;
- state and use the relationship between phase current and line current in star and delta configurations;
- compare the advantages and disadvantages of star and delta configurations;
- explain what is meant by 'rectification' and why it is often a necessary part of a three-phase system;
- distinguish between half-wave and full-wave rectification, and recognise them from voltage/time graphs;
- draw circuit diagrams for half-wave and full-wave rectification of a three-phase power supply;
- describe what is meant by 'ripple voltage' and explain the role of the smoothing capacitor in reducing it;
- distinguish between real, reactive and apparent power and state the units in which each is measured;
- use the formulae given to calculate real, reactive and apparent power;
- use traces of applied voltage and current to calculate phase angle and real, reactive and apparent power.

Instructor Guide

Introduction to Three-phase Power

What the student will need:

To complete the course, the student will need the following equipment:

LK5601	Lead, green 500mm, 4mm to 4mm stackable	2
HP3920	Three phase motor	1
HP4039	Tray Lid	1
HP5540	Deep tray	1
HP7750	Daughter tray foam cutout	1
HP8525	Crash foam	1
HP9390	Three phase power supply	1
HP9564	62mm daughter tray	1
LK2346	MES bulb, 12V, 0.1A	3
LK4025	Resistor, 10 ohm, 1W 5% (DIN)	2
LK5202	Resistor, 1k, 1/2W, 5% (DIN)	3
LK5243	Diode, power, 1A, 50V	6
LK5250	Connecting Link	10
LK5291	Lamp holder, MES	3
LK5603	Lead, red. 500mm, 4mm to 4mm stackable	2
LK5604	Lead, black, 500mm, 4mm to 4mm stackable	4
LK5607	Lead, yellow, 500mm, 4mm to 4mm stackable	2
LK5609	Lead, blue, 500mm, 4mm to 4mm stackable	2
LK5987	33uF non-electrolytic capacitor	1
LK6218	Resistor, 2.2k, 1/4W, 5% (DIN)	1
LK8900	7 x 5 metric baseboard with 4mm pillars	1
LK6529	Binding post	4

Order codes

UK LK4961
EU LK4961-EU
USA LK4961A-US

Using this course:

The experiments in this course should be integrated with teaching to introduce the theory behind it, and reinforced with written examples, assignments and calculations.

The worksheets should be printed / photocopied / laminated, preferably in colour, for the students' use. They should make their own notes, and carry out the tasks identified in the 'For your records' sections. They are unlikely to need their own permanent copy of the worksheets, but the instructor may choose to distribute copies of the Introduction for students' records.

Each worksheet has:

- an introduction to the topic under investigation;
- step-by-step instructions for the investigation that follows;
- a section headed 'So What', to collate and summarise results, offer extension work and encourage development of ideas, through collaboration with partners and with the instructor.
- a section headed 'For your records', to be copied and completed in students' exercise books.

This format encourages self-study, with students working at a rate that suits their ability. The instructor should monitor that students' understanding keeps pace with their progress through the worksheets. One way to do so is to 'sign off' each worksheet, as a student completes it, and in doing so have a brief chat with the student to assess grasp of the ideas involved in the exercises it contains.

Time:

It should take students between 5 and 7 hours to complete the worksheets. It is expected that a similar length of time will be needed to support the learning that takes place as a result.

Instructor Guide

Scheme of Work

Introduction to Three-phase Power

Worksheet	Notes for the Instructor	Timing
Introduction	<p>This course uses a number of devices which may be new to the student. The aim of the introduction is to present some information about them and how to use them.</p> <p>The third and fourth pages of the introduction focus on the Picoscope instrument, using version 6 of the software, but parts will be relevant to other types of oscilloscope and using other software.</p> <p>Depending on their ability and previous experience, some demonstrations of using the kit may be appropriate, in addition.</p> <p>Finally there is a discussion about AC power in its three aspects, real power, reactive power and true power. At some point, the instructor will need to reinforce these concepts through further teaching and examples.</p> <p>The instructor may choose to photocopy this introduction for each student.</p>	
1	<p>This worksheet acts as revision of work done earlier on single-phase AC, and introduces students to the three-phase generator and Picoscope.</p> <p>The latter may require an additional introduction by the instructor, depending on the students' experience of oscilloscopes and ADC-type instruments. This could include the significance of the timebase, voltage sensitivity and the use of triggering. The beauty of the Picoscope-type instrument is that it allows students to create and keep files showing the signals they encountered. The significance of 'pre-trigger' may need additional explanation. It allows the user to view a signal some time after triggering takes place.</p> <p>The instructor should encourage students to experiment with the Picoscope (or other oscilloscope) settings, as described in the 'Challenge' section, so that they feel more comfortable and confident in using the device.</p> <p>The 'So what' section examines the meaning of the terms 'amplitude', 'period' and frequency, and gives the formula relating the last two. The instructor should dwell on this and give examples of its use. This may be the time to practice the use of multipliers, especially 'milli' and 'kilo'.</p> <p>It also looks at the question of electrical power delivered by the supply. This section may prove difficult for some students. The instructor should test whether students have grasped its significance, perhaps through informal questioning. The relationship between r.m.s. and peak values given and students should work through examples using it. It is true only for sinusoidal signals. As the text says, it is best to think of r.m.s. as the equivalent DC voltage supply which would deliver the same power.</p> <p>The name 'root-mean square' comes from a mathematical treatment of the signal.</p> <ul style="list-style-type: none"> • Power can be calculated using the formula 'V^2/R'. • In this, negative and positive voltages both contribute equally, as any '-' signs disappear when squared. This is the 'square' term in r.m.s. • The voltage varies with time in a repeated pattern, so the power delivered is averaged over one cycle of the pattern (using calculus). This is the 'mean' term - another word for 'average'. • To get back to a voltage from the 'voltage squared' term, we take the square root of the quantity. Hence the 'root' part of r.m.s. <p>In the final section, students take measurements from traces of the sinusoidal signal to obtain amplitude, period and frequency. These can be obtained by using the 'measurement' and 'rulers' section of Picoscope, or with direct measurement. The instructor could have additional handouts with other traces on them to allow further practice.</p>	20 - 30 mins

Instructor Guide

Scheme of Work

Introduction to Three-phase Power

Worksheet	Notes for the Instructor	Timing
2	<p>The introduction to the worksheet sets out some advantages of three-phase power distribution over single-phase. In the 'For your records' section, students are asked to expand on this, using information gleaned from sources such as the internet. The instructor may wish to reinforce this with some formal teaching on the topic.</p> <p>The first part of the practical work is very quick, but well worth doing as it shows vividly what is happening in the three-phase supply. This is reinforced by use of the Picoscope, looking at higher frequency signals.</p> <p>Both versions of circuit symbol are found in literature. The first is useful in showing that three-phase can be treated as three separate sources of AC power. The second shows that three-phase power is often produced by three sets of coils inside a generator.</p> <p>Although the traces produced by the students are voltage/time graphs of the signals, it is often useful to use 'angle' rather than 'time' on the horizontal axis. The 'So what' section attempts to illustrate why this can be done. The instructor should ensure that the analogy works for the students.</p> <p>The important result is that the three phases of the supply are separated by phase angles of 120°. The 'So what section' obtains this result from the time difference between the phases. As before, the instructor should check that students understand this argument. More examples, using other frequencies and numbers of phases will help.</p>	25 - 35 mins
3	<p>In this worksheet, students use the current clamp for the first time. Although it measures currents as low as 10mA, electrical noise can make the trace indistinct and for that reason it is advisable to use as large a current as is feasible. The 100Ω 1W resistor allows an appreciable current without overheating (though it may get hot to the touch!) the height of the trace can be increased by coiling the wire from the generator to the resistor and trapping three or four turns of this coil inside the current clamp. (Not advisable if you are wanting to calculate the <i>amplitude</i> of the current!)</p> <p>There are two types of current clamp. Both rely on the magnetic fields that accompany any current flow. That magnetic field intensifies as the current increases and reverses when the current reverses. In one type, the jaws contain a coil of wire. A varying magnetic field induces a current in this coil (rather like the behaviour of a transformer.) This type is suitable only for AC measurement. The other type has a Hall effect sensor in the jaws. The magnetic field bends the current flow in the sensor, producing a voltage across the sensor that is a measure of the size (and indicates the direction) of the current under test. It can be used with AC or DC current measurement.</p> <p>The students are challenged to carry out the same investigation using a capacitor and then an inductor. Interpretation of the results is important as it reveals the phase relationships between voltage and current in these devices. Typical results are given in the 'So what' section.</p> <p>They can be explained as follows:</p> <ul style="list-style-type: none"> When an uncharged capacitor (i.e. voltage across it = 0V) is connected to a voltage source, there is an initial rush of charge onto the plates (i.e. the current is a maximum.) As the capacitor charges, the voltage across it rises, deterring further charge transfer (i.e. current falls.) Eventually, the capacitor is fully charged (i.e. voltage is maximum) and then no more charge transfer takes place (i.e. current = 0.) In other words, 'current leads voltage'. 	30 - 40 mins

Instructor Guide

Scheme of Work

Introduction to Three-phase Power

Worksheet	Notes for the Instructor	Timing
<p>3 continued...</p>	<ul style="list-style-type: none"> You can't have a current without a magnetic field, nor a magnetic field without a current so, rather like the chicken and the egg, which comes first? When an inductor is connected to a voltage source, (and so voltage is at its maximum,) even though there is very little (ohmic) resistance, no current flows, as there is no magnetic field. Slowly, the current and magnetic field build up. As they do so, an effect described by Lenz' law means that an opposing voltage builds up in the inductor coil. Current is increasing while voltage is decreasing. Eventually, current reaches a maximum, and at that point, net voltage is zero. Hence the phase angle! <p>Students could remember the word 'CIVIL' as a prompt for the phase rules: " In a Capacitor, current I leads voltage V, but current I lags behind in an inductor L."</p> <p>The 'So what' section then distinguishes between phase and line voltages. Students could be given the following definitions:</p> <ul style="list-style-type: none"> <i>Line voltage</i> - measured between any two lines in a three-phase system. <i>Phase voltage</i> - measured across a single component in a three-phase system. <i>Line current</i> - the current in any line between a source and load in a three-phase system. <i>Phase current</i> - the current in any component in a three-phase system. 	
<p>4</p>	<p>This worksheet tackles the issue of phasors and how to combine them. This topic needs a great deal of additional tuition by the instructor if the students are required to master the techniques.</p> <p>The investigation looks at driving the three-phase motor, initially using all three phases from the supply, and then using a single phase, with the help of a capacitor to excite a second coil with appropriate phase angle. Students are asked to compare its performance under each condition by (subjectively) sensing the torque produced. They also vary the supply frequency. At 150Hz, the motor cannot keep up with the rotating magnetic field, and so stops.</p> <p>In the 'So what' section, the concept of vectors is introduced along with the parallelogram rule for combining them. Here, this rule is applied by drawing a scale diagram, though mathematical methods can be applied instead. This rule allows physicists to manipulate quantities which have both a magnitude (size) and a direction, e.g. forces and velocities. However, in the case of AC electricity, the size and direction are changing continuously. Vector arithmetic is not enough! Instead, we use phasors. Like vector quantities, these use the length of an arrow to represent the size of the quantity and the direction of the arrow to indicate direction. However, the arrow rotates (anti-clockwise, by convention). The size and direction of the quantity at any instant is given by projecting the phasor onto the horizontal axis.</p> <p>In the example given, a series combination of resistor and capacitor, the same current flows through both, as they are in series. However, the voltage across the resistor is in phase with that current, whereas the voltage across the capacitor lags behind by a phase angle of 90°. Kirchhoff's 2nd law requires that the sum (in this case, vector sum) of the voltages across capacitor and resistor equals the supply voltage. This is shown in the diagram, which uses arbitrary lengths for the phasors. It is drawn at the instant when current reaches its maximum value (not that this matters.) It allows us to measure (or calculate) the phase angle between current and supply voltage. As stated above, students must work through a whole series of similar scenarios in order to feel competent in manipulating phasors.</p>	<p>30 - 40 mins</p>

Instructor Guide

Scheme of Work

Introduction to Three-phase Power

Worksheet	Notes for the Instructor	Timing
5	<p>The next two worksheets show the two configurations used for loads in three-phase systems, star (or 'Wye') and delta. The difference between them results in different relationships between line and phase voltages and line and phase currents.</p> <p>This investigation looks at these relationships for the star configuration. It requires that students be familiar with the use of multimeters to measure AC current and voltage. The instructor may wish to introduce some preliminary exercises to ensure that students can do this.</p> <p>The 'So what' section analyses results and compares them to the theoretical relationship. (This can be proved relatively easily using phasor diagrams and trigonometry, but here we just use the result of all that.)</p> <p>It includes a discussion of the term 'balanced load'. Essentially, there is no need for the return, neutral wire when the load is exactly balanced. The reason for this is that the three phases are not in phase. When one phase is positive, one of the others will be negative and will carry the current back to the three-phase source. This may need some emphasis by the instructor. The traces of the three-phase supply obtained in worksheet 2 may help with this explanation.</p> <p>The 'For your records' section includes a question as to why three-phase transmission systems usually use four wires, bearing in mind this last result. The answer lies in the reality that loads are not always balanced, in which case excess current is carried in the fourth neutral wire.</p>	25 - 40 mins
6	<p>This worksheet is a mirror-image of the last, but looking at the delta configuration.</p> <p>As previously, no attempt is made to derive the relationship between line and phase quantities. Students are simply asked whether their results support it. Previously, students connected the three-phase motor in star configuration. Now the challenge is to do so using a delta connection, and then to compare its performance. They should find that reversing two phases causes the motor to reverse rotation.</p> <p>Part of the 'For your records' section includes a comparison of the relative advantages of star and delta configurations.</p> <p>Possible topics include:</p> <ul style="list-style-type: none"> • the benefit of lack of a neutral wire in the delta system; • the ease of extracting a single-phase output from the star configuration; • the extra torque and self-starting ability for a three-phase motor in delta configuration; • the availability of two voltage values (line and phase) in star systems; the lack of an earthing point in delta systems ... <p>The instructor may choose to deliver this comparison or may set it as a research task for the students.</p> <p>Three-phase sources are usually connected in star configuration. If in delta, an unbalanced load would cause excess current to flow around the windings of the source, creating waste heat and possibly damaging the generator.</p> <p>It is quite common to find mixed systems, where the source is connected as a star and the load as a delta configuration.</p>	25 - 40 mins

Instructor Guide

Scheme of Work

Introduction to Three-phase Power

Worksheet	Notes for the Instructor	Timing
7	<p>There are good reasons for generating electrical power as AC - alternators are more efficient than equivalent DC generators, transformers can use AC but not DC... . However, most electronic devices require DC power. Fortunately, it is easy (and cheap) to convert AC to DC in a process called rectification (but relatively expensive to convert DC to AC!)</p> <p>Broadly speaking, there are two forms of rectification - half-wave and full-wave. This worksheet looks at half-wave rectification, the next at full-wave. The key to both is the one-way behaviour of diodes - offering very low resistance to current flow in one direction and very high resistance to flow in the other. (An alternative is to use thyristors, also called SCRs, silicon-controlled rectifiers, which also have this property.)</p> <p>Students capture oscilloscope traces that show that the supply to the load never crosses the zero volts line, and so is DC. The instructor may wish to emphasise the difference between DC and smooth DC, as this is certainly not smooth. A measure of smoothness is given by ripple voltage, discussed in the 'So what' section. This can be reduced by connecting a capacitor in parallel with the load. This acts as a reservoir of charge, driving current through the load in those periods when the current from the supply falls.</p>	25 - 40 mins
8	<p>This worksheet addresses full-wave rectification and begins with a reminder that vehicle alternators generate AC but then, internally, rectify it for use in the vehicle's DC electrical system.</p> <p>The investigation follows the same path as the previous one, first obtaining a full-wave rectified output and then looking at the effect of a smoothing capacitor. Unlike the previous one, it is not possible to view all three phases and the rectified output on the same trace because of the need to reference the three phases against the neutral terminal, but reference the output against the negative side of the load. Trying to do both at the same time results in a short-circuit of part of the system. The only way to do this is to use (expensive) 'differential' oscilloscope probes that are not automatically referenced to ground.</p> <p>The student is asked to investigate the effect of capacitor value, and of load resistance on the size of the ripple voltage. As before, the instructor should emphasise the importance of connecting electrolytic capacitors the right way round. The results should show that increasing the capacitor value reduces ripple (as it stores more charge and so can sustain the current for longer). Increasing the value of load resistance reduces the ripple because it draws a smaller current from the reservoir capacitor, allowing it to maintain the voltage longer.</p>	25 - 40 mins

Instructor Guide

Scheme of Work

Introduction to Three-phase Power

Worksheet	Notes for the Instructor	Timing
9	<p>The instructor may wish to direct the students back to the Introduction and its treatment of AC power. This ties in with earlier work on phasor diagrams and the meaning of rms quantities. All of this may prove difficult for some students and the instructor may need to offer substantial support to ease them through this.</p> <p>In the investigation, students build three systems, two using a single-phase power supply with a R-C and then a R-L network. Then they connect up the three-phase motor, in delta configuration, to the three-phase output from the generator.</p> <p>The best way to do this is to connect the three coils of the motor to each other in 'head-to-tail' fashion - U2 to V1, V2 to W1 and W2 to U1. Then the three-phases from the generator are connected to the 'nodes' U1, V1 and W1. The instructor may wish to check this wiring before students turn on the power supply.</p> <p>In all three cases, they obtain traces showing the relationship between applied voltage and current. In the case of the motor, this is done for one phase only (any phase). The motor is a balanced load and so the total power delivered is three times the power delivered to one phase.</p> <p>The 'So what' section shows how to obtain phase angle from the traces. There is likely to be considerable electrical noise on the current trace, because of its small amplitude. This makes determining the phase lag difficult, but we can still get a reasonable estimate. The instructor may wish to hand out traces which are free from noise to check that students are following the correct procedure.</p> <p>This is:</p> <ul style="list-style-type: none"> • Measure the distance between adjacent peaks on the voltage curve and between one voltage peak and the nearby current peak. These distances can then be converted into a phase angle. From there the power factor can be calculated. • Measure peak values for the voltage and current trace. The current clamp is set to the 20A range, which gives an output of 1mV for every 10mA of current, (see the Current Clamp Operator's Manual) and hence the peak value of current is calculated by multiplying the peakvalue of the current trace by 10. • Convert the peak values into rms values. • Apply the formulae to give the estimates of real and apparent power. <p>The 'For your records' section asks students to follow this procedure with the three traces they obtained in the investigation to obtain real and apparent power for these systems.</p>	40-55 mins

Instructor Guide

Scheme of Work

Introduction to Three-phase Power

Worksheet	Notes for the Instructor	Timing
10	<p>At crux of power factor correction is understanding that the most efficient way to deliver electrical power occurs when the applied voltage and resulting current are in phase with each other.</p> <p>This is illustrated in the first part of the investigation, using a resistive load. The resulting Picoscope traces should resemble the top diagram in the 'So what' section. The instructor should check that students interpret this correctly.</p> <p>The second part uses one coil of the three-phase motor as an inductive load. Obviously, the motor is not expected to rotate with this arrangement. The resulting traces should resemble the middle diagram in the 'So what' section, showing the current lagging behind the applied voltage. The students could be asked to identify those sections of the traces where power is being delivered to the load.</p> <p>In the third part, the large 33μF capacitor is connected in parallel with the inductive load. The effect is to pull the current drawn from the power supply back towards the applied voltage, increasing the power factor, in other words. As in the previous section, the students could be asked to identify sections where power is being delivered. In this way, the students should see that power is delivered over a bigger fraction of the AC supply cycle. Delivering the same amount of energy but doing it over longer times means that a smaller current can be used. Hence the improved efficiency though using power factor correction.</p> <p>The students are challenged to investigate the effect of changing the supply frequency. They should find that the best fit occurs at 150Hz.</p> <p>The instructor could set the task of researching power factor correction via the internet, to answer the first two tasks in the 'For your records' section. If this is done, it should be pointed out that we are not considering the effect of harmonics produced by non-linear loads such as diodes, which is treated in a different way.</p>	40-55 mins

Introduction to Three-phase Power

Revisions

03 08 16 Added last section on Power Factor Correction
 Added pages 5 and 6 on theory of Power Factor Correction